

B.TECH.**THEORY EXAMINATION (SEM–VI) 2016-17
INTRODUCTION TO ELECTRIC DRIVES****Time : 3 Hours****Max. Marks : 100****Note : Be precise in your answer. In case of numerical problem assume data wherever not provided.****SECTION – A****1. Explain the following:****10 x 2 = 20**

- (a) What are the necessary conditions for turning-on of an SCR?
- (b) Are the turn-on and turn-off times of a thyristor constant? On what factors do these depend?
- (c) Discuss why the method of power flow control is called phase controlled converter method when power flow from a 1-phase source to load R can be controlled through the use of a thyristor.
- (d) What are the advantages of single phase bridge converter over single phase mid-point converter?
- (e) What is meant by TRC?
- (f) Why diodes should be connected in anti parallel with the thyristors in inverter circuits?
- (g) Write few advantages of using cyclo converter for synchronous motor speed control.
- (h) What are the main disadvantages of armature resistance control?
- (i) Define dynamic braking.
- (j) Write methods of starting of synchronous motor.

SECTION – B**2. Attempt any five of the following questions:****5 x 10 = 50**

- (a) Explain turn off characteristics of thyristors. List out the name of Thyristor triggering methods.
- (b) Explain the V-I characteristics of Thyristor. Also explain Latching current and Holding Current.
- (c) Justify the statement “free wheeling diode improves the power factor of the system.”
- (d) Derive the expressions of a 1- ϕ full wave bridge rectifier fully controlled for $R-L-E$ load for: (i) Continuous load current (ii) Discontinuous load current. Also draw suitable waveforms.
- (e) Explain the operation of 3- ϕ half wave controlled full wave rectifier with desired waveforms.
- (f) What is chopper? Explain the working and control strategies of chopper with suitable waveforms.
- (g) Enumerate the various methods of speed control of 3- ϕ induction motor when fed through semiconductor devices.
- (h) Describe the slip recovery control scheme.

SECTION – C**Attempt any two of the following questions:****2 x 15 = 30**

- 3 Explain the working of 120° mode of 3- ϕ inverter with relevant waveforms of phase and line voltages and compare it with 180° mode inverter.
- 4 Define the principle of operation of cycloconverter. Explain the working of 1- ϕ :
 - (i) Step down,
 - (ii) Step up cycloconverter.

- 5 An armature of a separately excited dc motor is fed from 1- ϕ full wave fully controlled converter. The supply ac voltage $V = 220\text{Volts}$, $R_a = 0.5\Omega$ and motor constant is $K = 0.4\text{ V-s/rad}$. For load torque of 20 Nm at 1500 rpm and for constant armature current, calculate;
- (i) Firing angle of the converter,
 - (ii) Rms value of thyristor current,
 - (iii) Input power factor of the motor.