

B.TECH
(SEM VII) THEORY EXAMINATION 2022-23
FILTER DESIGN

Time: 3 Hours**Total Marks: 100**

Note: Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief.**2 x 10 = 20**

- (a) Why we use Analog Filters?
- (b) Give few applications of Op-amp.
- (c) What are passive elements?
- (d) Define frequency response.
- (e) What is the use of band pass filters?
- (f) Give few applications of Integrators.
- (g) What is the difference between first order and second order filters.
- (h) Define low pass filter.
- (i) What is the Chebyshev polynomial?
- (j) How do you find the Chebyshev coefficient?

SECTION B

2. Attempt any three of the following:**10 x 3 = 30**

- (a) Explain the working of Non-Inverting operational amplifiers. Also give its applications.
- (b) What is frequency transformation in filter design? How can you obtain a band pass filter from given low pass filter at normalized frequency?
- (c) What is a Butterworth low pass filter? How do you calculate the order of a Butterworth filter?
- (d) What do you understand by filters with arbitrary transmission zeros. What are poles in Butterworth filter?
- (e) What is an Elliptic / Cauer Filter? Give few advantages and applications of Cauer filters.

SECTION C

3. Attempt any one part of the following:**10 x 1 = 10**

- (a) What is a filter? Why it is important? Explain ideal response and response of practical filter.
- (b) Explain Op-amp. Discuss the application of Op-amp resistor circuits.

4. Attempt any *one* part of the following:

10 x 1 = 10

- (a) Explain with suitable example; how you can convert a low pass filter into a band stop filter using frequency transformation?
- (b) The IC 741 is connected as non-inverting amplifier with closed loop gain of 20. Calculate its bandwidth.

5. Attempt any *one* part of the following:

10 x 1 = 10

- (a) Draw the magnitude response and pole location diagram of all the second order filters.
- (b) Discuss biquads filters. Explain how the frequency response of a biquads filter can be calculated?

6. Attempt any *one* part of the following:

10 x 1 = 10

- (a) Explain the frequency warping in Bilinear transformation.
- (b) What are the main features of Butterworth filters? Explain cascade design.

7. Attempt any *one* part of the following:

10 x 1 = 10

- (a) What is inverse Chebyshev filter? What are properties of Chebyshev filter?
- (b) What are the characteristics of Elliptical Response? Compare it with Chebyshev and inverse Chebyshev response.

QP23DP1_290 | 09-01-2023 13:33:23 | 117.55.242.132