

Paper Id: 

2	3	1	9	1	0
---	---	---	---	---	---

Roll No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B.TECH.**  
**(SEM VII) THEORY EXAMINATION 2022-23**  
**VLSI DESIGN**

**Time: 3 Hours****Total Marks: 100****Note:** Attempt all Sections. If you require any missing data, then choose suitably.**SECTION A**

- 1. Attempt all questions in brief. 2x10 = 20**
- Define the term critical path.
  - State the term sheet resistance.
  - Define the term Scaling.
  - What is a delay in any circuit?
  - What is a cascade circuit?
  - Differentiate between Combinational and Sequential circuits.
  - What is a semiconductor memory?
  - Define the term Low-Power circuit.
  - Define the term defects.
  - What is the term testability?

**SECTION B**

- 2. Attempt any three of the following: 10x3 = 30**
- Explain different design methodologies used in VLSI Design.
  - Describe linear delay model used in VLSI Design.
  - What is noise in VLSI? Define different noise margins used to analyse and circuit.
  - Describe different types of Power dissipation in VLSI circuits.
  - Explain different faults defined in any VLSI circuits.

**SECTION C**

- 3. Attempt any one part of the following: 10x1 = 10**
- Describe MOORE'S Law. Give a detailed evolution of VLSI Circuits.
  - Explain the Y-Chart VLSI design flow by describing each arm separately.
- 4. Attempt any one part of the following: 10 x1 = 10**
- Describe the term Logical effort and calculate the logical effort of a CMOS 2-input NOR gate.
  - Define different types of Scaling used in VLSI Design.
- 5. Attempt any one part of the following: 10x1 = 10**
- With a neat diagram make the layout of a 2-input AND gate using CMOS.
  - Describe the working and applications np-CMOS logic.
- 6. Attempt any one part of the following: 10x1 = 10**
- Explain the working and applications of a 6-T SRAM cell.
  - Describe different types of ROM cells.
- 7. Attempt any one part of the following: 10x1 = 10**
- With the use of a block diagram, define the Ad-HoC technique for testing a VLSI Circuit.
  - Describe Built-in-Self-Test technique for testing a VLSI Circuit.